

Ohms Law The current flowing **through** a *resistor* at a constant temperature is directly proportional to the voltage **across** the resistor. So, if you double the voltage, the current also doubles.

$$I = \frac{V}{R}$$


Key Skills

- ⇒ Soldering
- ⇒ Fault finding
- ⇒ CAD/CAM

Circuit diagrams are special drawings that use symbols and other conventions (rules) to describe circuits.

LED's (Light Emitting Diode)

Advantages	Disadvantages
Power efficient	Cost
Long life	Drive circuit
Low temperature	Directional
Hard to break	
Small	
Fast turn on	

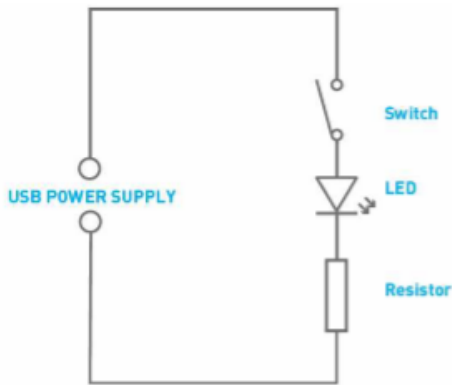


Tools - Circuit construction

PRECISION DRILL UNIT	
SOLDERING IRON	
SOLDERING IRON HOLDER	
SIDE CUTTERS	
WIRE STRIPPERS	
SOLDER (LEADED)	

Key Vocabulary

Input	The part of a system or circuit that takes something in, e.g. a sensor, switch or input socket
Process	The central part of a system or circuit that changes the input(s) in some way, e.g. amplifies it
Output	The end of the system or circuit that could be the generation of light, sound or movement
Current	The flow of electricity, measured in AMPs. This can be likened to the flow of water.
Voltage	The amount of energy (push) behind the flow of electricity. Measured in VOLTS.
Power	The voltage multiplied by the current, measured in WATTS
Resistance	The opposite to flow. A reduction in the flow of electricity through part of a circuit or component. Measured in OHMS (Ω).

RESISTOR COLOUR CODE

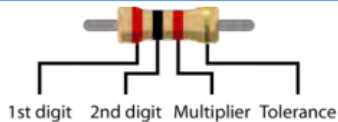

1st BAND	2nd BAND	3rd BAND (NUMBER OF ZEROS)	TOLERANCE (ACCURACY RANGE)
			GOLD - 5%
0	0	0	
1	1	1	
2	2	2	
3	3	3	
4	4	4	
5	5	5	
6	6	6	
7	7	7	
8	8	8	
9	9	9	

EXAMPLES: RED, RED, RED = 2200 OHMS (R or Ω)
 YELLOW, VIOLET, BROWN = 470 OHMS (R or Ω)

